# Variable Gain Amplifier

# MitchElectronics® 2019



## www.mitchelectronics.co.uk

# CONTENTS

Schematic ... 3 How It Works ... 4 Materials ... 5 Construction ...6 Important Information ... 7 T&C ... 8

## **SCHEMATIC**



#### Schematic (Blocktised)



Variable Gain Amplifier

# SCHEMATIC EXPLANATION

The Variable Gain Amplifier is a simple circuit that uses an LM358 to provide a non-inverting amplifier with an adjustable gain. The circuit uses a 4-way DIP switch to allow multiple gains and settings and these settings are shown in the table below

| DIP SW 1 | DIP SW 2 | DIP SW 3 | DIP SW 4 | Function      |
|----------|----------|----------|----------|---------------|
| 1        | 0        | 0        | 0        | Gain = 2      |
| 0        | 1        | 0        | 0        | Gain ≈ 4      |
| 0        | 0        | 1        | 0        | Gain ≈ 7      |
| 0        | 0        | 0        | 1        | Gain 1 to 100 |

The table above shows the gain of the four main stages but what happens if you enable more than one setting? In this situation there will be multiple resistances in parallel and when combined with the potentiometer you can achieve fine gain tuning. The gain of the amplifier can be calculated using the formula below

Gain = 
$$1 + \frac{R_2}{R_1}$$
 where  $R_1 = 100$  and  $R_2 = R1, R2, R3, or RV1$ 

The potentiometer has a resistance range of  $0\Omega$  to  $10K\Omega$  which provides a wide range of gain values between 1 to 100 but beware that gain values above 20 are effectively unusable due to the inherent limitations in op-amps. The op-amp U1A is connected to a non-inverting unity gain buffer to improve the output impedance and ensure that output devices cannot affect the gain stage of the Variable Gain Amplifier.

# Note : The maximum output voltage of the LM358 is VCC—1.5V. This means that if powered by 5V then the maximum output voltage will be 5—1.5 = 3.5V!

The Variable Gain Amplifier also has a switch SW2 which is used to configure the circuit as either a dual rail amplifier or a single rail amplifier. When closed, the circuit shorts the VSS and GND pins together to make the amplifier work on single rails (those that are only + and - such as a battery). When open, the circuit can work with dual rails that include a positive, negative, and ground and this is useful in many analog circuits such as audio.

# MATERIALS

| Component                           | Component Name | Quantity | Looks like |
|-------------------------------------|----------------|----------|------------|
| LM358                               | U1             | 1        |            |
| 8 DIP Socket                        | U1             | 1        |            |
| 100Ω Resistor                       | R1, R4         | 2        |            |
| 330Ω Resistor                       | R2             | 1        |            |
| 680Ω Resistor                       | R3             | 1        |            |
| 10KΩ Potentiometer                  | RV1            | 1        |            |
| 100nF Capacitor                     | C1, C2         | 2        |            |
| 4 Way DIP Switch                    | SW1            | 1        |            |
| Slide Switch                        | SW2            | 1        |            |
| Red, Blue, Green, and<br>Black Wire | -              | 1        |            |
| РСВ                                 | -              | 1        |            |

#### Check that you have the following components

## CONSTRUCTION

#### **Download the electronics construction manual**

To learn how to construct circuits on PCBs download the Electronics Construction Manual from Mitch-Electronics using the link below. This document shows you how to install all electronic components used in MitchElectronics kits. The list below shows the sections relevant to this kit so do not worry if you see component sections in the document that don't come with this kit!

www.mitchelectronics.co.uk/electronicsConstructionManual.pdf

#### **Relevant sections in the electronics construction manual**

Resistors

Capacitors

ICs

Switches

**Potentiometers** 

Wires

#### Colour 1<sup>ST</sup>Band 2<sup>ND</sup>Band 3<sup>RD</sup>Band Multiplier Tolerance BLACK 0 0 1Ω 1st Significant Digit 10Ω BROWN 2nd Significant Digit Multiplier 1kΩ ORANG 10kO YELLOW 4 4 4 1 - First Digit 104 0 - Second Digit BLUE 6 6 1MO ±0.25% 10MΩ 4 - 10000 Multiplier VIOLET ±0.10% ±0.05% GREY 8 8 8 100nF Capacitor WHITE 7 7 7 GOLD ±10% SILVER 4 Band Resistor 5.6k ±5%

#### **RESISTOR AND CAPACITOR IDENTIFICATION**

# **IMPORTANT INFORMATION**



# **TERMS AND CONDITIONS**

#### **MitchElectronics Mission**

The main goal of MitchElectronics products is to provide safe electronics to makers and professionals alike while keeping the cost affordable. MitchElectronics kits are ideal for classrooms whereby students can learn about electronics using a hands-on approach which is not only highly effective at teaching students but also improves hand-eye co-ordination as well as grow interest in electronics. Since MitchElectronics kits are aimed at novices and those who are new to electronics they are designed to use low voltage power supplies such as 9V batteries which are inherently safe due to their limited voltage and current capabilities.

#### **MitchElectronics Liability**

MitchElectronics kits must be inspected and tested by a competent individual before use and must be constructed by those who are competent to do so. MitchElectronics is not liable for kits and products that are constructed incorrectly or to a poor standard whereby poor standard includes (but not limited to) poor solder connections, overheated components, and damaged components. MitchElectronics is not liable for harm, injury, or damage caused by the misuse of kits and/or products if

- Incorrectly constructed
- Powered by sources other than "portable batteries" or the specified power supply
- Kits used outside their operational range (such as voltage supply, temperature etc.)
- Used as a sub-system (i.e. connected to additional circuits and modules)
- Used in a non-educational environment
- Used in a commercial environment
- Used in any dangerous or potentially hazardous environment
- Purchased from an unauthorised third party

Portable batteries refers to low powered alkali batteries. Lithium-based batteries and those with large current capabilities (such as lead-acid batteries) are not considered portable or safe

The use of the kits or products in the above scenarios automatically voids any warrantee or guarantee of that kit or product.

#### Kits must be

- Inspected for damage before and after construction
- Inspected for missing parts
- Constructed correctly by a qualified individual
- Used in an appropriate manner (i.e. within operational ranges)
- Purchased from an authorised seller

Those who are not competent to construct, inspect, and test kits and products must be accompanied by a competent individual and that competent individual assumes all responsibility for harm or damages and MitchElectronics is not liable for any harm or damage.

#### **Missing Parts**

MitchElectronics is only liable for missing parts for kits that have been purchased within 28 days and that have been purchased directly from www.mitchelectronics.co.uk. MitchElectronics is not liable for any product sold by an unauthorised third party.